Jeong-Yeol Yoon

Introduction to Biosensors

From Electric Circuits to Immunosensors

Springer

Contents

1	Introduction	1
1.1	Sensors	1
1.2	Transducers	2
1.3	Biosensors	4
1.4	Bioreceptors	5
1.5	Transducers for Biosensors	11
1.6	Overview of this Textbook	12
	Bibliography	14
2	Resistors	15
2.1	Electric Circuit	15
2.2	Current and Voltage	15
2.3	Resistance and Ohm's Law	17
2.4	Resistors in Series, or Voltage Divider	18
2.5	Potentiometer, or Pot	19
2.6	Resistors in Parallel, or Current Divider	20
2.7	Laboratory: Resistors	22
2.7.1	Reading Resistor Values	22
2.7.2	Breadboards	24
2.7.3	Connecting to a Power Supply	25
2.7.4	Resistance Measurements	27
2.7.5	Task 1: Resistors in series	28
2.7.6	Task 2: Resistors in parallel	30
2.7.7	Task 3: "Droop"	31
2.7.8	Potentiometer (Pot)	33
2.8	Further Study: Thévenin's theorem	35
	Bibliography	37
3	Diodes and Transistors	39
3.1	Semiconductors	39
3.2	Diodes	40

3.3	Zener Diode	43
3.4	Transistors	44
3.5	Laboratory: Diodes and Transistors	49
3.5.1	Operational Amplifier	49
3.5.2	Task 1: LED	50
3.5.3	Task 2: Zener Diode	53
3.5.4	Task 3: Transistor	55
	Bibliography	57
4	Temperature Sensors	59
4.1	Thermocouple	59
4.2	Thermistor	60
4.3	Diode Temperature Sensor	62
4.4	Transistor Temperature Sensor	64
4.5	Laboratory: Temperature Sensors	65
4.5.1	Task 1: Thermistor	65
4.5.2	Task 2: Zener Diode Temperature Sensor	66
4.5.3	Task 3: Transistor Temperature Sensor	69
	Bibliography	73
5	Wheatstone Bridge	75
5.1	Wheatstone Bridge	75
5.2	Strain Gauge	77
5.3	Cantilever Biosensor	78
5.4	Laboratory: Wheatstone Bridge	79
5.4.1	Task 1: Wheatstone Bridge	79
5.4.2	Task 2: Wheatstone Bridge for a Thermistor	81
5.4.3	Task 3: Wheatstone Bridge for a Strain Gauge	84
	Bibliography	85
6	Op-amp	87
6.1	Op-amp	87
6.2	Basics of Op-amp	89
6.3	Voltage Follower or Buffer Op-amp	90
6.4	Non-inverting Op-amp	91
6.5	Inverting Op-amp	92
6.6	Summing Op-amp	93
6.7	Differential Op-amp	94
6.8	Laboratory: Op-amp	95
6.8.1	Task 1: Non-inverting Op-amp Operation	95
6.8.2	Task 2: Signal Conditioning for Temperature Sensor	98
	Bibliography	101

7	Light Sensors	103
7.1	Light	103
7.2	Photoresistor	104
7.3	Photodiode	105
7.4	Phototransistor	108
7.5	Light Emitting Diode	109
7.6	Laser Diode	111
7.7	Laboratory: Photodiode	113
7.7.1	Task 1: Photoconductive Operation	113
7.7.2	Task 2: Photovoltaic Operation	116
	Bibliography	119
8	Spectrophotometry and Optical Biosensor	121
8.1	Spectrophotometry	121
8.2	Miniature Spectrophotometer	124
8.3	Optical Glucose Sensor	126
8.4	Laboratory: Glucose Sensor	128
8.4.1	Task 1: Glucose Assay Kit with a Spectrophotometer	129
8.4.2	Task 2: Glucose Assay Kit with LED/PD Circuit	134
8.5	Further Study: Pulse Oximeter	137
	Bibliography	138
9	Fluorescence and Optical Fiber	141
9.1	Fluorescence	142
9.2	Fluorescent Dyes	144
9.3	Optical Fibers	147
9.4	Laboratory: Optical Fiber Spectrometer	150
9.4.1	Reflection Probe	151
9.4.2	SpectraSuite™ Software	152
9.4.3	Task 1: Fluorescent Lamp Measurement	153
9.4.4	Task 2: Fluorescent Excitation and Emission Measurement	155
	Bibliography	160
10	Electrochemical Sensors	161
10.1	Electrolytic and Electrochemical Cells	161
10.2	Ion-Selective Electrodes (Potentiometric)	166
10.3	pH Electrode (Potentiometric)	167
10.4	Electrochemical Glucose Sensor (Amperometric)	168
10.5	Conductometric Biosensors	170
10.6	Laboratory: pH Meter and Glucose Meter	171
10.6.1	Buffer	171
10.6.2	Task 1: Buffer Preparations and Their pH Measurements	172

10.6.3	Task 2: pH Meter Circuit	175
10.6.4	Task 3: Commercial Electrochemical Glucose Sensor	178
	Bibliography	180
11	Piezoelectric Sensors	181
11.1	Piezoelectricity	181
11.2	Pressure Sensors	183
11.3	Crystal Oscillators	184
11.4	Quartz Crystal Microbalance	184
11.5	Viscoelasticity Consideration in QCM	187
11.6	Flow-Cell QCM as Biosensor	189
11.7	Laboratory: Quartz Crystal Microbalance	190
11.7.1	Task 1: Quantifying BSA Adsorption on QCM Sensor	190
	Bibliography	197
12	Immunosensors	199
12.1	Enzyme-Linked Immunosorbent Assay	199
12.2	Antibodies	202
12.3	Antibody Fragments and Aptamers	203
12.4	Lateral-Flow Assay	206
12.5	Optical Immunosensors	207
12.6	Surface Plasmon Resonance Immunosensor	209
12.7	Electrochemical Immunosensors	210
12.8	Impedance Immunosensors: Interdigitated Microelectrode Immunosensor	212
12.9	Piezoelectric Immunosensors: QCM Immunosensor	213
12.10	Immunosensing Kits Versus Handheld Immunosensors	214
12.11	Laboratory: ELISA kit	215
12.11.1	Task 1: Insulin ELISA Kit	215
12.11.2	Task 2: Insulin ELISA Kit with Optical Fiber Spectrometer	217
12.11.3	Task 3: Insulin ELISA Kit with Cell Phone Camera	219
12.12	Further Study: DNA Sensors	221
	Bibliography	222
13	Lab-on-a-Chip Biosensors	225
13.1	What Is Lab-on-a-Chip	225
13.2	How to Make an LOC: Photolithography and Soft Lithography	227
13.3	Early LOC: Capillary Electrophoresis	231
13.4	LOC for Point-of-Care Testing	232
13.5	Use of Optical Fibers in LOC	235
13.6	Sample/Reagent Introduction	236

Contents	xiii
13.7 Mixing in LOC	238
13.8 LOC with Cell Phone Camera	239
13.9 Other Applications of LOC	239
13.10 Laboratory: Lab-on-a-Chip	240
13.10.1 Task 1: LOC Fabrication	241
13.10.2 Task 2: Mixing Experiment	243
13.11 Further Study: Latex Immunoagglutination Assay in LOC	245
13.12 Further Study: Polymerase Chain Reaction in LOC	247
Bibliography	252
Index	257